

# Gen IMS II Homework 1

Yiping Deng

February 8, 2018

## Task 1

a)

Starting from the basic formula, we have:

$$Q = CV_C \quad (1)$$

$$\frac{dQ}{dt} = i \quad (2)$$

$$V_S = V_C + V_R \quad (3)$$

$$V_R = iR \quad (4)$$

Using the formula above, we can differentiate (1) with respect to t

$$\frac{dQ}{dt} = C \frac{dV_C}{dt} = i \quad (5)$$

$$(6)$$

Thus, equation (4) can be substituted using (5)

$$V_R = RC \frac{dV_C}{dt} \quad (7)$$

Plug into (3), we have first order seperable ODE

$$RC \frac{dV_C}{dt} + V_C = V_S \quad (8)$$

b)

We can solve (9) by seperation of variable:

$$RC \frac{dV_C}{V_C - V_S} = -dt \quad (9)$$

Integrate both side, we have

$$\ln(V_C - V_S) = -\frac{t}{RC} + \text{constant} \quad (10)$$

Take the exponential function on both side

$$V_C - V_S = Be^{-\frac{t}{RC}} \quad (11)$$

Also, plug-in the initial condition, we have:

$$0 - V_S = B \quad (12)$$

$$B = -V_S \quad (13)$$

The solution is:

$$V_C(t) = V_S - V_S e^{-\frac{t}{RC}} \quad (14)$$

$$A = V_S \quad (15)$$

$$B = -V_S \quad (16)$$

$$\lambda = -\frac{1}{RC} \quad (17)$$

$$(18)$$

c)

Using the following python code, we can generate a graph

```
import numpy as np
import matplotlib.pyplot as plt
import math
```

```
def graph(formula, points):
    x = points
    y = formula(x)
    plt.plot(x, y)
    plt.show()
```

```
graph(lambda t: 10 - 10 * np.exp(-t/(1000 * 100* 10**-6)), np.linspace(0, 0.7, 200))
```

